

Instruction ROM Design – 16 × 8

1 Introduction

Objective

Design, implement and simulate a **16-word × 8-bit Read-Only Memory (ROM)** to serve as the program / lookup memory for a soft microcontroller core.

Why it's important

Every CPU fetches instructions from non-volatile memory. A small on-chip ROM is perfect for boot code, fixed lookup tables, or microcode in resource-constrained FPGA/ASIC designs.

2 Functional Specifications

Signal	Width	Dir.	Description
in_address	4	Input	Address from Program Counter (0 – 15)
out_instructions	8	Output	Instruction / data stored at in_address

Parameter	Purpose	Default
Depth	Number of locations	16
Width	Bits per location	8

3 Theory of Operation

1. **Random-access read-only array** – contents fixed at synthesis.
2. Address (in_address) acts as an index; data is returned combinatorially.
3. In a real microcontroller, the Program Counter increments each cycle, feeding sequential addresses to the ROM.
4. Because the ROM is pure combinational logic (no clock), access latency = one propagation delay.

4 Example Walk-Through

in_address (PC)	Stored Instruction (out_instructions)	Mnemonic*
0000	0001 0010	LOAD R1, #2
0001	0010 0101	ADD R1, R5
0010	0011 0110	SUB R1, R6
0100	0101 0001	OR R0, R1
0111	1000 0010	JMP 2

5 Verilog RTL Code

```
module rom (  
    input [3:0] in_address,    // 4-bit address (0-15)  
    output [7:0] out_instructions // 8-bit instruction  
);  
  
    // 16 × 8 ROM  
    reg [7:0] mem [15:0];  
  
    // Hard-coded contents (example program)  
    initial begin  
        mem[0] = 8'b0001_0010; // LOAD R1, #2  
        mem[1] = 8'b0010_0101; // ADD R1, R5
```

```

mem[2] = 8'b0011_0110; // SUB  R1, R6
mem[3] = 8'b0100_0011; // AND  R0, R3
mem[4] = 8'b0101_0001; // OR   R0, R1
mem[5] = 8'b0110_0010; // XOR  R0, R2
mem[6] = 8'b0111_0000; // NOT  R0
mem[7] = 8'b1000_0010; // JMP  2
mem[8] = 8'b1001_0001; // JZ   1
mem[9] = 8'b1010_0000; // STORE R0, MEM
mem[10] = 8'b1011_0011; // LOAD  R3, MEM
mem[11] = 8'b1100_0000; // NOP
mem[12] = 8'b1101_0000; // HALT
mem[13] = 8'b0000_0000; // Reserved
mem[14] = 8'b0000_0000; // Reserved
mem[15] = 8'b0000_0000; // Reserved
end

```


```

// Combinational read
assign out_instructions = mem[in_address];

```

endmodule

RTL:-

 

TESTBENCH:-

```

`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 07/05/2025 06:55:00 PM
// Design Name:
// Module Name: tb
// Project Name:

```


```
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////
```

```
module tb;
reg [3:0]address;
wire [7:0]out_instructions;

rom uut(
.in_address(address),
.out_instructions(out_instructions));

initial begin
repeat (20) begin
address = $random %16;
#10;
end
end
endmodule
```

7 Simulation Results

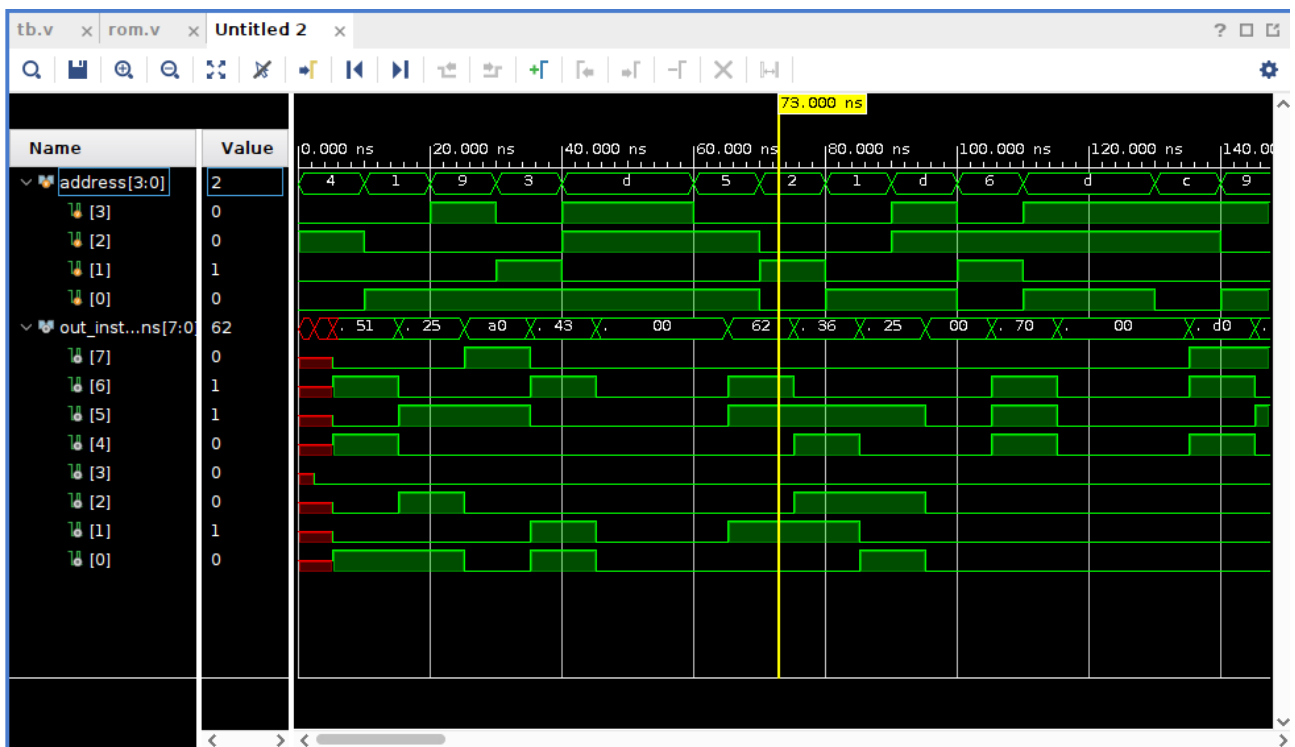

8 Applications

- **Instruction ROM** in a home-built 8-bit microcontroller
- **Lookup tables:** sine/cosine, CRC polynomials, font glyphs
- **Microcode storage** for complex CISC instructions
- **Boot ROM / reset vectors** in embedded systems

9 Conclusion

- Created and verified a **16×8 combinational ROM**, the first permanent memory block in the MCU project.
- Demonstrated correct address-to-data mapping in simulation.
- Next step: hook this ROM to a Program Counter and build the Instruction Decoder.